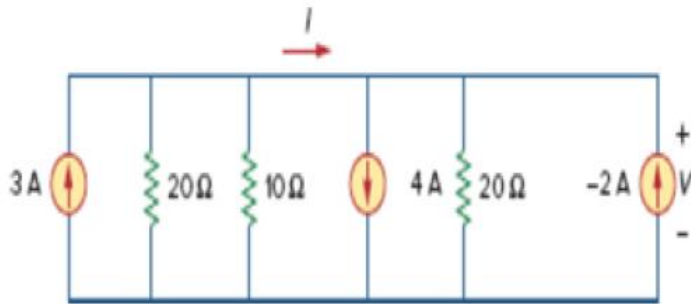


## Homework #2 Solutions

### Problem 2.18

Find  $I$  and  $V$  in the circuit of Fig. shown below.



### Solution.

*Step 1.* We can make use of both Kirchhoff's KVL and KCL. KVL tells us that the voltage across all the elements of this circuit is the same in every case. Ohm's Law tells us that the current in each resistor is equal to  $V/R$ . Finally we can use KCL to find  $I$ .

Applying KCL and summing all the current flowing out of the top node and setting it to zero we get,  $-3 + [V/20] + [V/10] + 4 + [V/20] - [-2] = 0$ .

Finally at the node to the left of  $I$  we can write the following node equation which will give us


$$I - 3 + [V/20] + [V/10] + I = 0.$$

*Step 2.*  $[0.05 + 0.1 + 0.05]V = 0.2V = 3 - 4 - 2 = -3$  or  $V = -15$  volts.

$$I = 3 - V[0.05 + 0.1] = 3 - [-15]0.15 = 5.25 \text{ amps.}$$
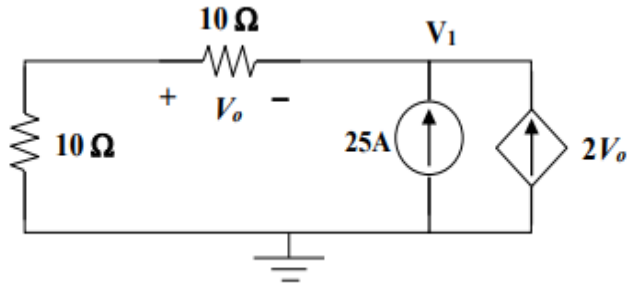
### Problem 2.22

Find  $V_o$  in the circuit in Fig. below and the power absorbed by the dependent source.



### Solution:

At the node, KCL requires that  $[-V_o/10] + [-25] + [-2V_o] = 0$  or  $2.1V_o = -25$

or  $V_o = -11.905 \text{ V}$

The current through the controlled source is  $i = 2V_o = -23.81 \text{ A}$

and the voltage across it is  $V_1 = (10+10) i_o$  (where  $i_o = -V_o/10$ )  $= 20(11.905/10) = 23.81 \text{ V}$ .


Hence,

$P_{\text{dependent source}} = V_1(-i) = 23.81 \times (-(-23.81)) = 566.9 \text{ W}$

Checking,  $(25-23.81)^2 (10+10) + (23.81)(-25) + 566.9 = 28.322 - 595.2 + 566.9 = 0.022$  which is equal zero since we are using four places of accuracy!
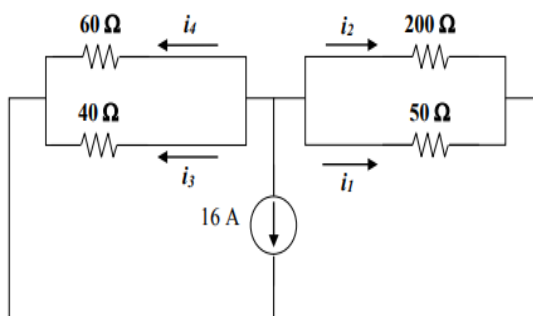
### Problem 2.32

Find  $i_1$  through  $i_4$  in the circuit in Fig. below.



### Solution

We first combine resistors in parallel.

$$40 \parallel 60 = \frac{40 \times 60}{100} = 24 \, \Omega \text{ and } 50 \parallel 200 = \frac{50 \times 200}{250} = 40 \, \Omega$$

Using current division principle,


$$i_1 + i_2 = \frac{24}{24 + 40}(-16) = -6 \text{ A}, i_3 + i_4 = \frac{40}{64}(-16) = -10 \text{ A}$$

$$i_1 = \frac{200}{250}(6) = -4.8 \text{ A and } i_2 = \frac{50}{250}(-6) = -1.2 \text{ A}$$

$$i_3 = \frac{60}{100}(-10) = -6 \text{ A and } i_4 = \frac{40}{100}(-10) = -4 \text{ A}$$
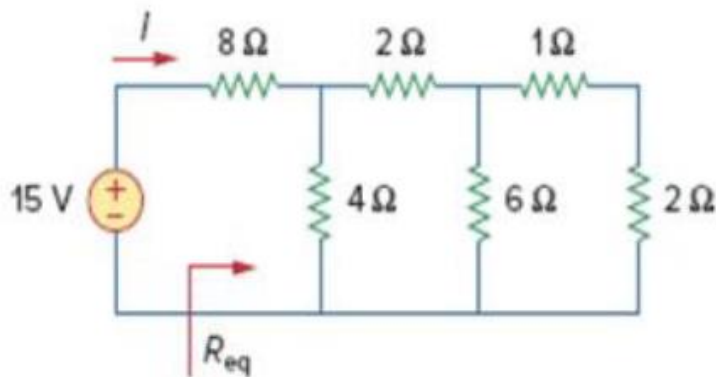
### Problem 2.40:

For the ladder network shown below, find  $I$  and  $R_{eq}$ .



### Solution 2.40


$$R_{eq} = 8 + 4 \parallel (2 + 6 \parallel 3) = 8 + 2 = 10 \, \Omega$$

$$I = \frac{15}{R_{eq}} = \frac{15}{10} = 1.5 \text{ A}$$

**Problem 2.56:** Determine  $V$  in the circuit shown below.

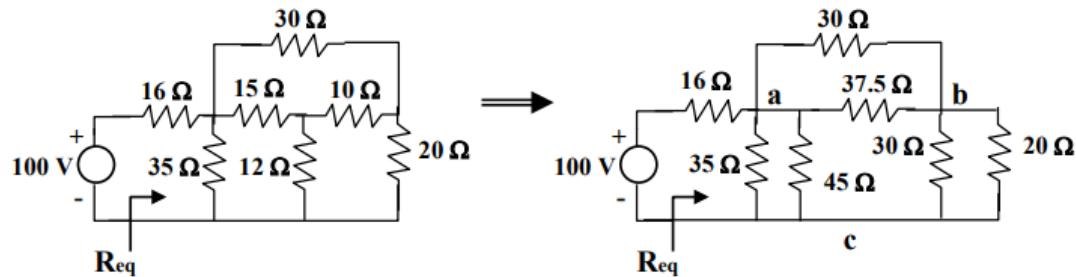**Solution:**

We need to find  $R_{eq}$  and apply voltage division. We first transform the Y network to  $\Delta$



$$R_{ab} = \frac{15 \times 10 + 10 \times 12 + 12 \times 15}{12} = \frac{450}{12} = 37.5 \Omega$$

$$R_{ac} = 450/(10) = 45 \Omega, R_{bc} = 450/(15) = 30 \Omega$$

Combining the resistors in parallel,

$$30 \parallel 20 = (600/50) = 12 \Omega,$$

$$37.5 \parallel 30 = (37.5 \times 30 / 67.5) = 16.667 \Omega$$

$$35 \parallel 45 = (35 \times 45 / 80) = 19.688 \Omega$$


$$R_{eq} = 19.688 \parallel (12 + 16.667) = 11.672 \Omega$$

By voltage division,

$$v = \frac{11.672}{11.672 + 16} 100 = \underline{\underline{42.18 \text{ V}}}$$

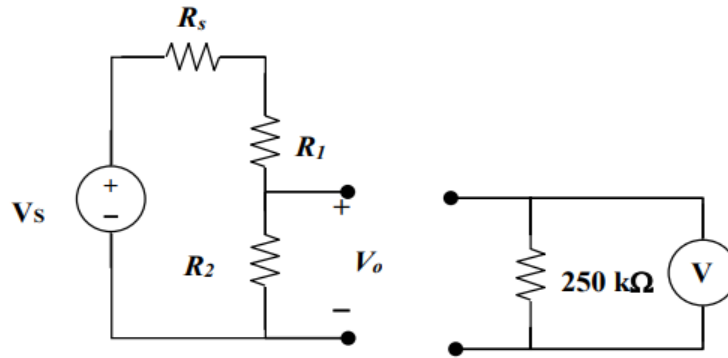**Problem 2.69**

A voltmeter is used to measure  $V_o$  in the circuit in Fig. 2.129. The voltmeter model consists of an ideal voltmeter in parallel with a 250-kΩ resistor. Let  $V_s = 95 \text{ V}$ ,  $R_s = 25 \text{ k}\Omega$ , and  $R_1 = 40 \text{ k}\Omega$ . Calculate  $V_o$  with and without the voltmeter when (a)  $R_2 = 5 \text{ k}\Omega$  (b)  $R_2 = 25 \text{ k}\Omega$  (c)  $R_2 = 250 \text{ k}\Omega$



**Solution:**

$$\text{Step 1.} \quad V_o = V_s \frac{\left( \frac{250kR_2}{250k + R_2} \right)}{R_s + R_1 + \frac{250kR_2}{250k + R_2}} = 95 \frac{\left( \frac{250kR_2}{250k + R_2} \right)}{65k + \frac{250kR_2}{250k + R_2}} \text{ and}$$

$$V_o = V_s \frac{R_2}{R_s + R_1 + R_2} = 95 \frac{R_2}{65k + R_2}.$$

$$\text{Step 2.} \quad \text{(a) } V_o = 95 \frac{\left( \frac{250kR_2}{250k + R_2} \right)}{65k + \frac{250kR_2}{250k + R_2}} = 95(4.902/69.902) = \mathbf{6.662 \text{ volts}} \text{ and}$$

$$V_o = 95 \frac{R_2}{65k + R_2} = 95(5k/70k) = \mathbf{6.786 \text{ volts}}$$

$$(b) V_o = 95 \frac{\left( \frac{250kR_2}{250k+R_2} \right)}{65k + \frac{250kR_2}{250k+R_2}} = 95(22.727/87.727) = \mathbf{24.61 \text{ volts}}$$
 and

$$V_o = 95 \frac{R_2}{65k+R_2} = 95(25/90) = \mathbf{26.39 \text{ volts}}$$

$$(c) V_o = 95 \frac{\left( \frac{250kR_2}{250k+R_2} \right)}{65k + \frac{250kR_2}{250k+R_2}} = 95(125/190) = \mathbf{62.5 \text{ volts}}$$
 and

$$V_o = 95 \frac{R_2}{65k+R_2} = 95(250/315) = \mathbf{75.4 \text{ volts}}$$